

## Anderson's bridge

**Aim** :- To measure the self - inductance of a given coil by Anderson's bridge method.

**Apparatus** :- Inductor, standard capacitor, resistors ( fixed resistances and variable pots as given in the circuit ) signal generator, head phones and connecting terminals.

**Formula** :- Inductance of given coil  $L = C [ ( R_1 + R_2 ) R_5 + R_2 R_4 ]$  mH

Where     C = Capacity of the standard capacitor (  $\mu$  F )  
                $R_2, R_3, R_4$  = Known, fixed and non – inductive resistances ( K $\Omega$  )  
                $R_1, R_5$  = Variable resistances ( K $\Omega$  )

**Description** :- Anderson's bridge is the most accurate bridge used for the measurement of self – inductance over a wide range of values, from a few micro-Henries to several Henries. In this method the unknown self-inductance is measured in terms of known capacitance and resistances, by comparison. It is a modification of Maxwell's L - C bridge. In this bridge, double balance is obtained by the variation of resistances only, the value of capacitance being fixed.

**Procedure** :-The circuit diagram of the bridge is as shown in the figure. The coil whose self-inductance is to be determined, is connected in the arm AB, in series with a variable non-inductive resistor  $R_1$ . Arms BC, CD and DA contain fixed and non – inductive resistors  $R_2$ ,  $R_3$  and  $R_4$  respectively. Another non - inductive resistor  $R_5$  is connected in series with a standard capacitor C and this combination is put in parallel with the arm CD. The head - phones are connected between B and E. The signal generator is connected between A and C junctions.

Select one capacitor and one inductor and connect them in appropriate places using patch chords. The signal generator frequency is adjusted to audible range. A perfect

balance is obtained by adjusting  $R_1$  and  $R_5$  alternatively till the head – phones indicate a minimum sound. The values of  $R_1$  and  $R_5$  are measured with a multi-meter( While measuring the  $R_1$  and  $R_5$  values, they should be in open circuit ).In the balance condition the self – inductance value of the coil is calculated by using the above formula. The experiment is repeated with different values of C.

**Precautions** : - 1) The product ( $CR_2R_4$ ) must always be less than L .


2)  $R_1$  and  $R_5$  are adjusted until a minimum sound is heard in head – phones.

**Result** :-

---

**Table**

S.No.	Capacity ( C ) μ F	Resistance ( R <sub>1</sub> ) Ω	Resistance ( R <sub>5</sub> ) Ω	Calculated value (L) $C [ ( R_1 + R_2 ) R_5 + R_2 R_4 ]$ mH	Standard value of L mH
1.					
2.					
3.					
4.					
5.					
6.					

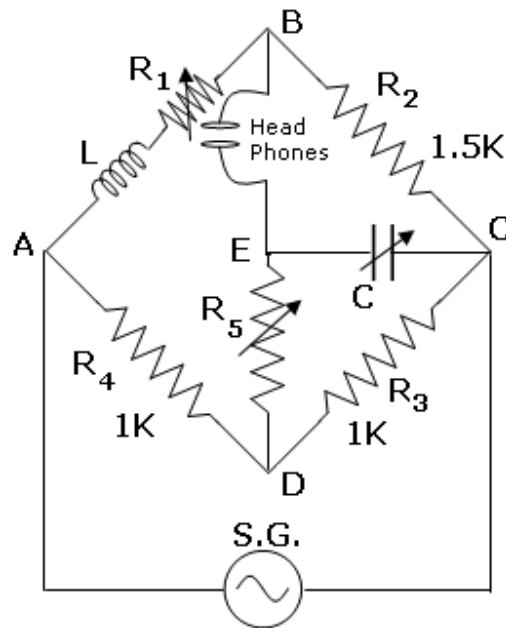

\*\*\*\*\*