

## De Sauty's bridge

**Aim** :- To compare the capacities of two condensers (or) to find the capacitance of the given condenser, by using De Sauty's bridge.

**Apparatus** :- Two condensers, two resistance boxes or two resistance pots of 10 KHz, Signal generator, head phone and well insulated connecting wires.

**Formula** :- Capacity of a unknown capacitor  $C_2 = \frac{R_1}{R_2} \times C_1 \mu\text{F}$

Where  $C_1$  is the capacity of the known capacitor.

$R_1$  and  $R_2$  are the variable non- inductive resistors.

**Description** :- The De Sauty's bridge is an A.C Bridge works on the principle of Wheat stone's bridge . This bridge is used to determine the capacity of an unknown capacitor  $C_2$  in terms of the capacity of a standard known capacitor  $C_1$ . Here  $R_1$  and  $R_2$  are non - inductive resistors .  $R_1, R_2, C_1$  and  $C_2$  are connected in a Wheat stone's bridge as shown in the figure-1. When the bridge is balanced, the ratios of impedances are equal as given below.

$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$$

$$\frac{1}{j\omega C_1} = \frac{1}{j\omega C_2} \times \frac{R_1}{R_2}$$

$$\frac{C_2}{C_1} = \frac{R_1}{R_2}$$

**Procedure** :- The connections are made as shown in the figure. The resistance  $R_1$  and a condenser  $C_1$  are in series in one branch of the bridge and a resistance  $R_2$  and another capacitor  $C_2$  are in series in another branch. The A.C signal generator frequency is adjusted to a fixed value of 1 KHz or below, which is convenient to our ear.

A resistance is unplugged in  $R_1$  and the resistance  $R_2$  is adjusted till the sound in the head - phone is reduced to zero level . The value of  $R_2$  is measured with a multi-meter and noted. While measuring the resistances, they should be in open circuit. The above process is repeated for different values of  $R_1$  and the values are noted in the table .

When the hum in the head – phone is at zero level , then the time constants of the upper and the lower braches of Wheat stone’s bridge equal i.e.  $C_1R_1 = C_2R_2$  .

$$C_2 = \frac{R_1}{R_2} \times C_1 \mu\text{F}$$

**Precautions** :- 1) The connecting wires should not be in contact with the experiment table.


2) The wires are checked up for continuity .

Result :-

---

**Table**

S.No.	Capacity of known condenser $C_1 \mu F$	Resistance $R_1 \Omega$	Resistance $R_2 \Omega$	Capacity of unknown condenser $C_2 = \frac{R_1}{R_2} \times C_1 \mu F$	Standard Value of $C_2 \mu F$
1.					
2.					
3.					
4.					
5.					
6.					

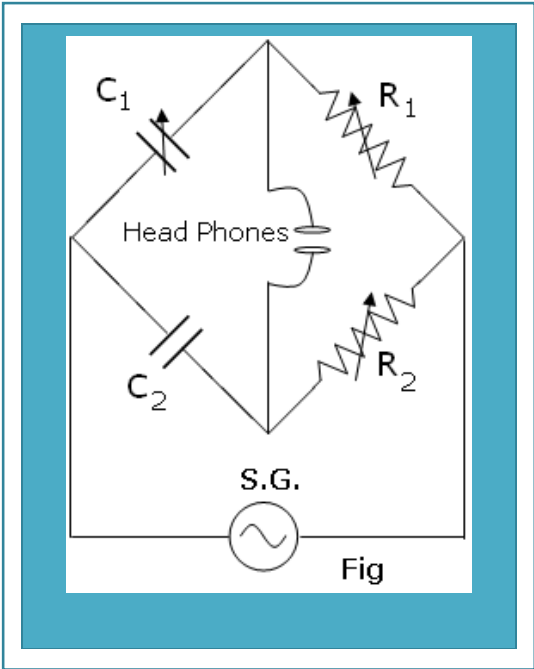

\*\*\*\*\*