

## Operational Amplifier as inverting amplifier

**Aim** :- To compare the experimental voltage gain of the operational amplifier with that of the theoretical value and also to observe the in put and the out put are out of phase.

**Apparatus** :- Operational amplifier ( IC 741 ), C.R.O., signal generator, power supply to the amplifier, non inductive resistors of different values and connecting terminals.

**Formula** :-

$$\frac{e_o}{e_i} = - \frac{R_f}{R_i}$$


Where  $e_i$  and  $e_o$  are in put and out put voltages (peak to peak voltages in C.R.O.)

$R_i$  and  $R_f$  are in put and feed back resistors.

**Description** :- The heart of an analog computer is the Operational Amplifier. The Operational Amplifier is a stable, high gain DC coupled amplifier which is widely used with a large amount of negative feed back. Many important mathematical operations such as signal addition (or subtraction), differentiation, integration, comparison, isolation, amplification, oscillators, arbitrary function generators etc. are performed in analog computer by using Op-Amp.

An ideal Operational Amplifier would have very high open loop gain, bandwidth and zero noise, off set and drift. The basic circuit block of the amplifier is shown in the Fig. as a triangle with 3 signal terminals. Any signal fed to the inverting input terminal (marked '-') appears amplified at the output with reverse phase, while signal fed to the non-inverting input (marked '+') appears amplified at the output without phase reversal. Now for ideal amplifier in which the input impedance is infinite, no current is drawn from the signal source, and the difference in potential between two input terminals is zero due to infinite gain. But non-ideal amplifier has high voltage gain in the range from  $10^3$  to  $10^7$  and input impedance is high and of the order of millions of ohms. So these two conditions are satisfied in the case of non-ideal amplifier also. The amplifier does not distort the waveform of the input voltage regardless of the frequency component. In practice, however, the band width of operational amplifier (namely the range of frequencies of input signal over which A is constant) extends from 0 Hz to few MHz. As the gain of the amplifier equals A at 0 Hz, the amplifier is called direct coupled.

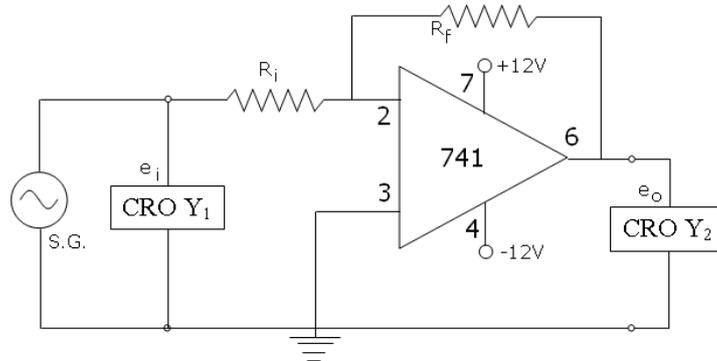**Theory** :-Operational Amplifier has odd number of stages for obtaining negative feed back, Since for performing various mathematical operations we need negative feed back.



Inverting amplifier (Fig)

Now from Fig. we can derive closed loop gain (i.e. gain with feed back) for an Operational Amplifier, in the Fig  $R_f$  is Feed back Resistor. Now applying Kirchoffs current law at place  $e_g$ .

We get

$$\frac{e_i - e_g}{R_i} = \frac{e_g - e_o}{R_f} \text{ ----- (1)}$$

OR

$$\frac{e_i}{R_i} + \frac{e_o}{AR_i} = \frac{-e_o}{AR_f} - \frac{e_o}{R_f} \text{ ----- (2)}$$

As per the operational amplifier  $e_o = -Ae_g$  and putting  $e_g = -e_o/A$

OR

$$e_o \left( \frac{1}{AR_i} + \frac{1}{AR_f} + \frac{1}{R_f} \right) = - \frac{e_i}{R_i}$$

$$\frac{e_o}{R_f} \left( \frac{R_f}{AR_i} + \frac{1}{A} + 1 \right) = - \frac{e_i}{R_i}$$

Now  $R_f/R_i$  is of the order of 1 to 10 &  $A = 10^6$ .

$\therefore \frac{R_f}{AR_i}$  and  $1/A$  can be neglected.

There fore the above equation becomes

$$\frac{e_o}{R_f} = - \frac{e_i}{R_i}$$

OR

$$\frac{e_o}{e_i} = - \frac{R_f}{R_i}$$

The ratio  $= R_f / R_i$  must not exceed 10. The reason is that greater will be ratio, lesser will be precision. We also see that the output voltage depends only upon the input voltage and values of the two passive components, namely, the resistors. This implies that the precision by the mathematical operation performance depends only on the precision of the externally connected passive components.

**Procedure** :- The phase terminal of the signal generator is given to the inverting input (2) of the Op. Amp. IC 741 through an input resistor  $R_i$ . The other terminal of the signal generator and the non-inverting terminal (3) of the amplifier are grounded. The output (6) of the amplifier is fed back to the input (2) through a feedback resistor  $R_f$ . To measure the I/P and O/P voltages, the signal generator phase terminal and the output (6) of the amplifier are given to  $Y_1$  and  $Y_2$  plates of the CRO respectively. The other terminals of the CRO are grounded. The terminals 7 and 4 of the op. amp. are connected to +12V and -12V of the power supply.

First the input resistor  $R_i$  (nearly  $1K\Omega$ ), feedback resistor  $R_f$  (nearly  $2K\Omega$  to  $10K\Omega$ ) values and input voltage  $e_i$  (0.1V to 0.5V) are fixed. Then observe the input and output signals on CRO screen. Adjust the time base and vertical gain (volts/div.) of the  $y_1$  and  $y_2$  plates to a convenient value, such that the two signals are stationary and completely observable. Adjust the frequency of the input signal such that input and output signals are out of phase. Measure the input and output voltages  $e_i$  and  $e_o$  (vertical peak to peak) and note the values in the table. The experiment is repeated by changing the values of  $R_i$  and  $R_f$ .

The theoretical gain ( $R_f/R_i$ ) and experimental gain ( $e_o/e_i$ ) are calculated and compared in the table.

**Precautions** :- 1. Output of Op. Amp. Can not beyond 15V if so, the Op. Amp. Will go in to saturation state. So do not feed input more than 1.5 V.

2. Adjust the input frequency such that input and output signals are out of phase.
3. Check the continuity of the connecting terminals before connecting them.
4. See that the ratio  $= R_f / R_i$  should not exceed 10

**Result** :-

---

**Table**

S. No.	$R_i$ $\Omega$	$R_f$ $\Omega$	Input voltage ( $e_i$ )			Out put Voltage ( $e_o$ )			Gain	
			Peak to peak (Vertical) (Divisions) (n)	Voltage Sensitivity. (Volt/Div) (d)	Voltage ( $e_i$ )= $n \times d$ (volts)	Peak to peak (Vertical) (Divisions) (n)	Voltage Sensitivity. (Volt/Div) (d)	Voltage $e_o = n \times d$ (volts)	Theoretical ( $R_f/R_i$ )	Experimental ( $e_o/e_i$ )